

复位按钮

3V3

R1 10kΩ

RESET

SW1

C7 1uF

GND

TS-1010-C-A

U3

GND

3V3

EN

IO1

IO2

TXD0

RXD0

IO4

IO15

IO16

IO17

IO18

IO19

IO20

IO3

IO46

IO9

IO10

IO11

IO12

IO13

IO14

IO45

IO48

IO47

IO21

IO14

IO01 I2C SDA

IO02 I2C SCL

U0TXD

U0RXD

IO42 LCD BL

IO41 LCD SCK

IO40 LCD MOSI

IO39 LCD DC

IO38 I2S MCK

NC

NC

NC

IO0 BOOT

IO45 I2S DO

IO48 U2TXD

IO47 U2RXD

SE PWM0

IO14 I2S BCK

4G UART0 RXD

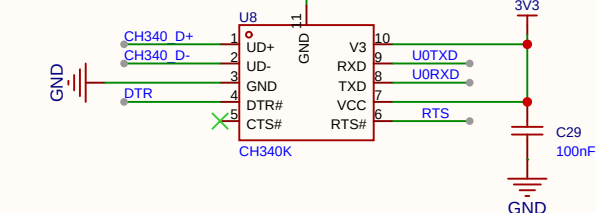
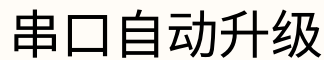
4G UART0 TXD

确认都是1.8V电平?

K230 GPIO45 RX

K230 GPIO44 TX


2.4GHz

[illegible]

The top diagram shows the connection of the SY8088AAC chip to an AU_3V3 supply. The chip is connected to the supply via a series of capacitors (C16, C17, C18) and a resistor (R19). The chip's EN pin is connected to GND, and its LX pin is connected to GND. The chip's FB pin is connected to the supply via a resistor (R22). The chip's IN pin is connected to the supply via a resistor (R24). The chip's OUT pin is connected to the supply via a resistor (R24). The chip's GND pin is connected to GND.


The bottom diagram shows the connection of the SY8088AAC chip to a 3V3 supply. The chip is connected to the supply via a series of capacitors (C21, C22, C23) and a resistor (R53). The chip's EN pin is connected to GND, and its LX pin is connected to GND. The chip's FB pin is connected to the supply via a resistor (R54). The chip's IN pin is connected to the supply via a resistor (R55). The chip's OUT pin is connected to the supply via a resistor (R55). The chip's GND pin is connected to GND.

IO扩展

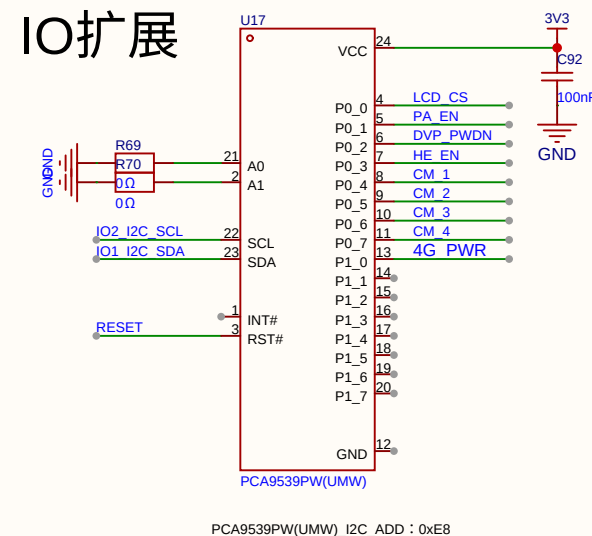


原理图	Schematic1			创建日期	2026-07-19
板子	Board1			更新日期	2026-08-08
绘制		New Project_2026-07-19_11-10-43			
审阅					
		版本	尺寸	页 1 共 6	
		V1.0	A4	嘉立创EDA	


音频ADC

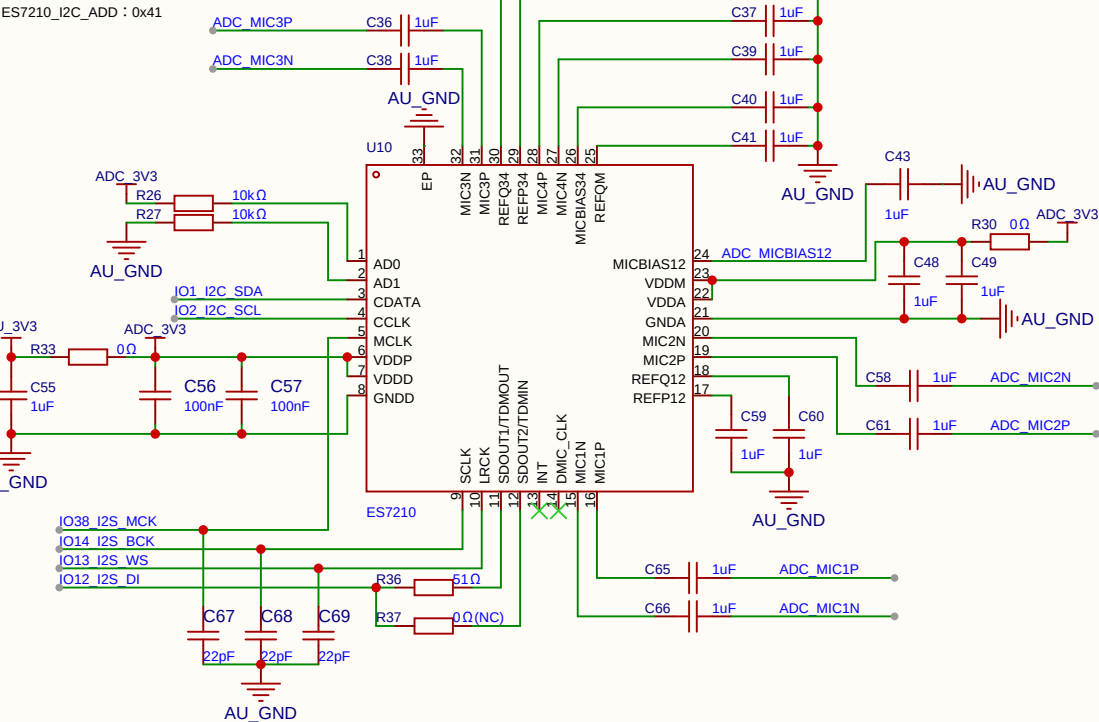


音频Codec

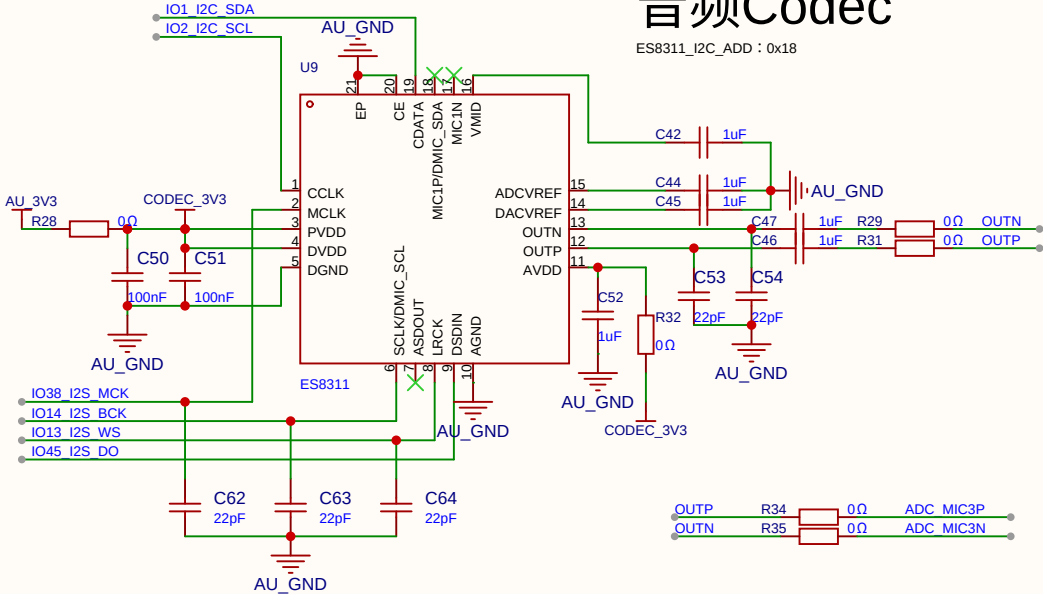

麦克风



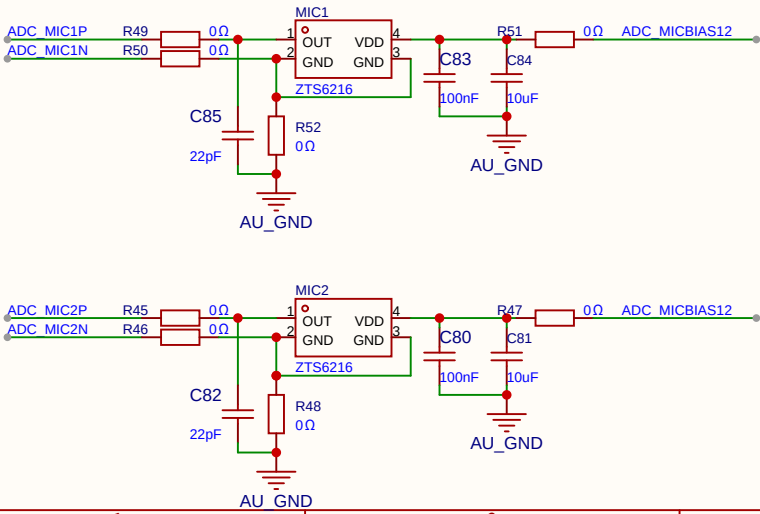


音频功放

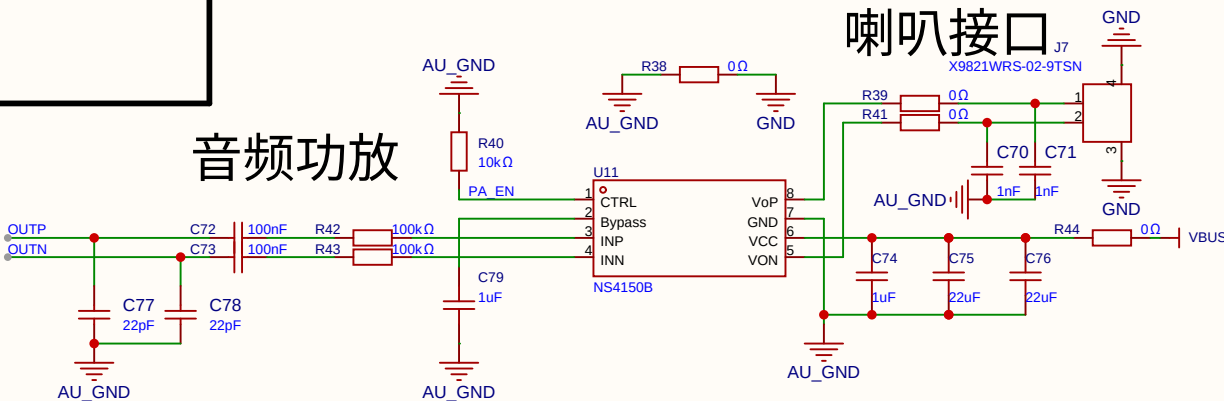


喇叭接口


原理图	Schematic1		创建日期	2026-07-23
板子	Board1		更新日期	2026-07-23
绘制			图页	咪头，喇叭
审阅			New Project_2026-07-19_11-10-43	
		版本	尺寸	页 2 共 6
		V1.0	A4	嘉立创EDA

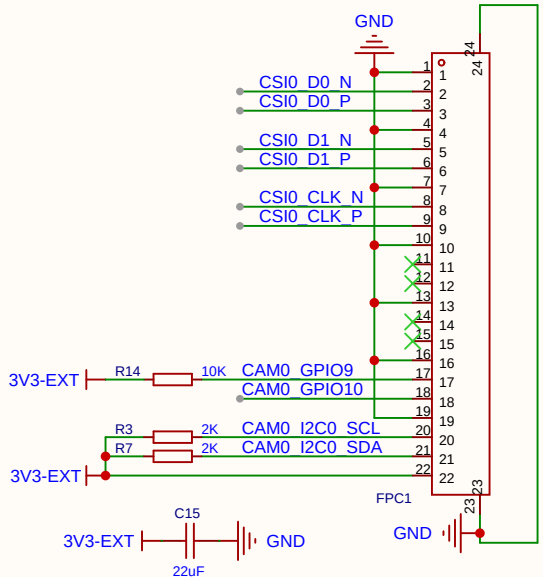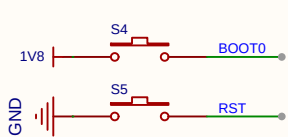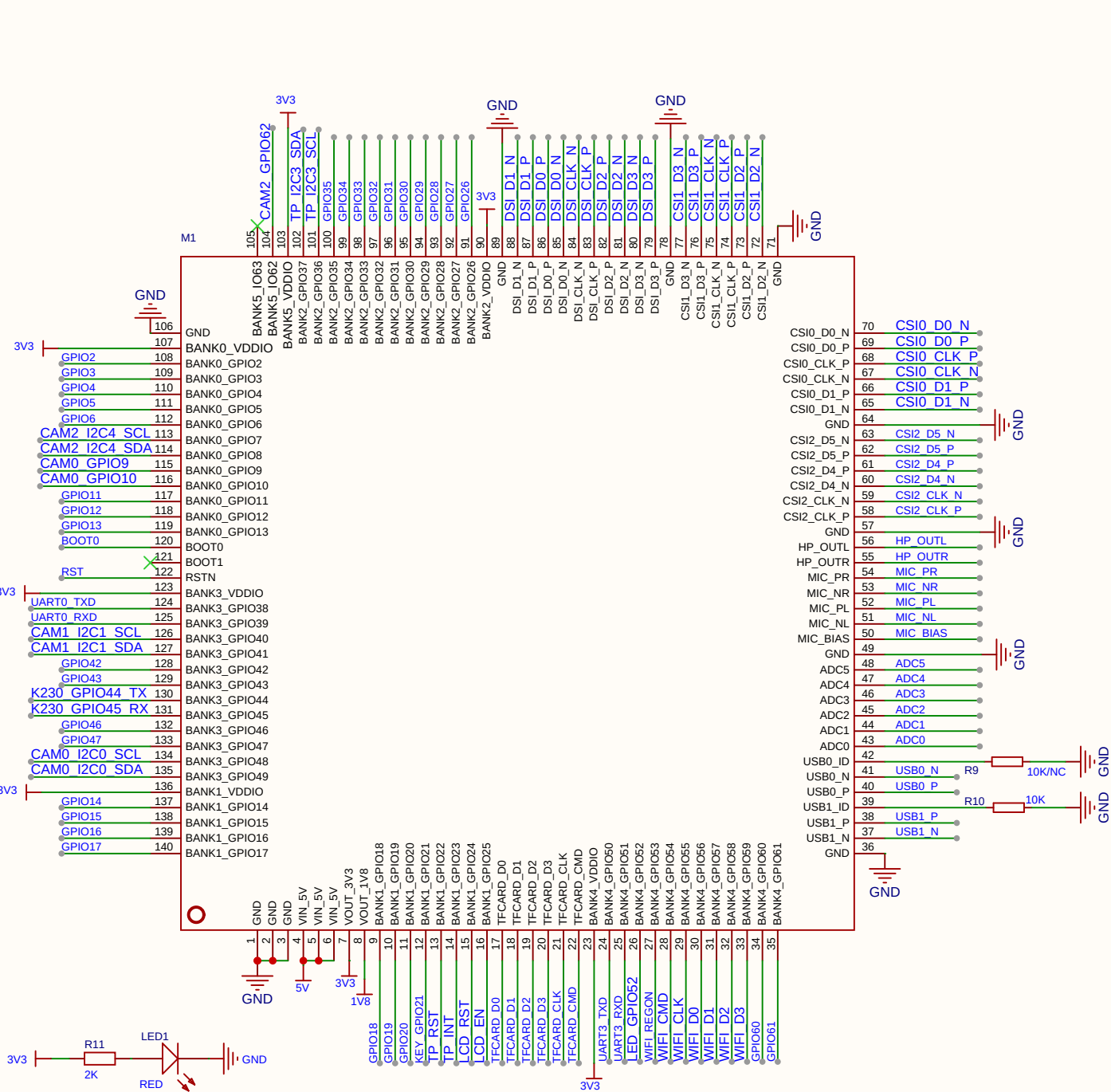

摄像头


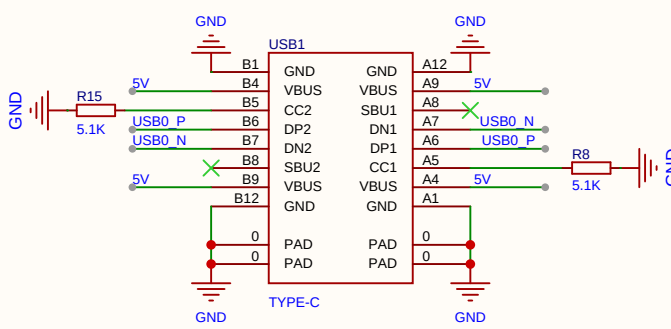


TYPE-C

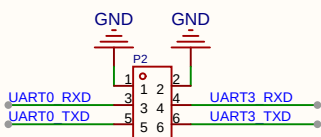

调试


CM-K230

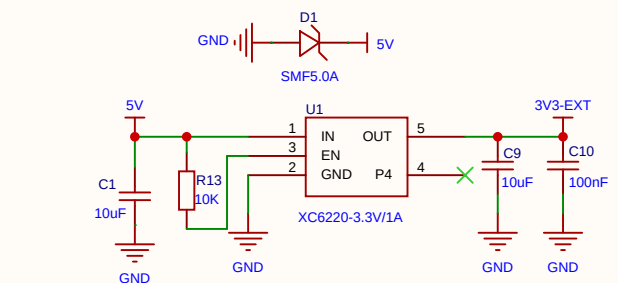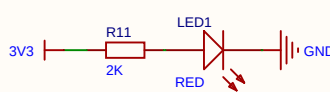


External 3.3V

原理图	Schematic1			创建日期	2026-07-23
				更新日期	2026-08-08
板子	Board1			图页	K230
绘制				New Project_2026-07-19_11-10-43	
审阅					
		版本	尺寸	页 3 共 6	
嘉立创EDA		V1.0	A4	嘉立创EDA	


4G电源

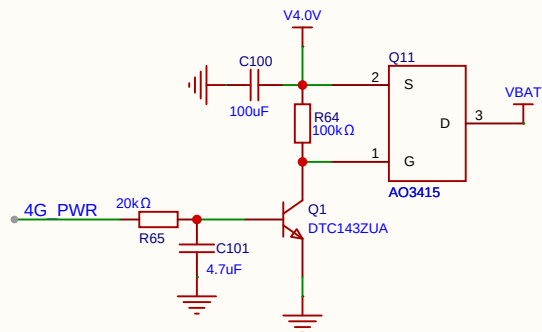


ML307A

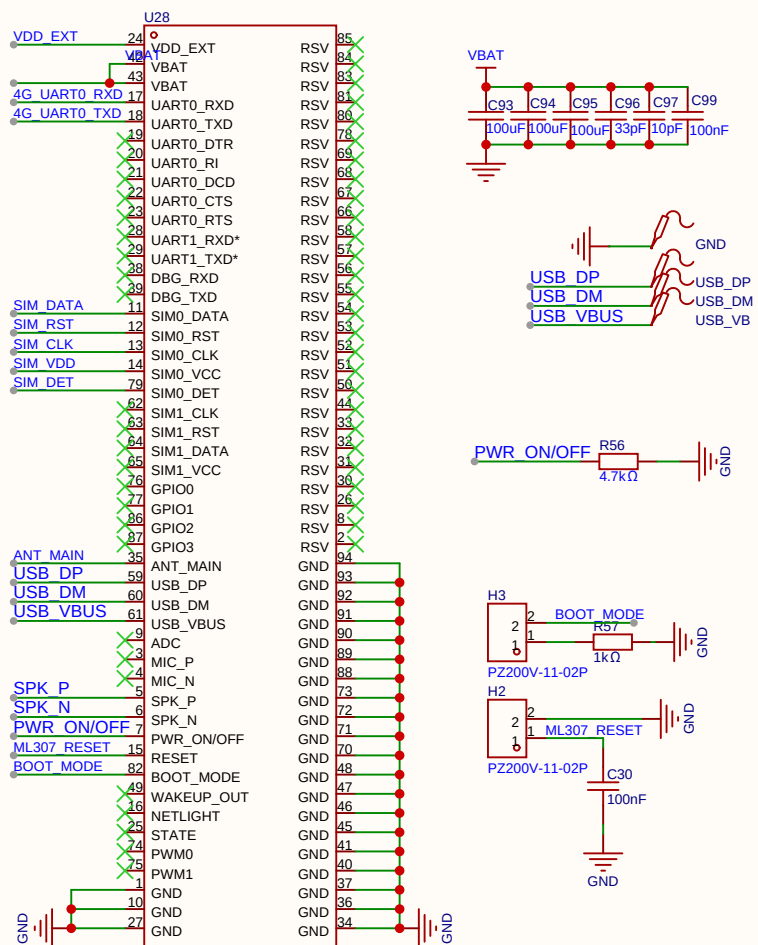

SIM

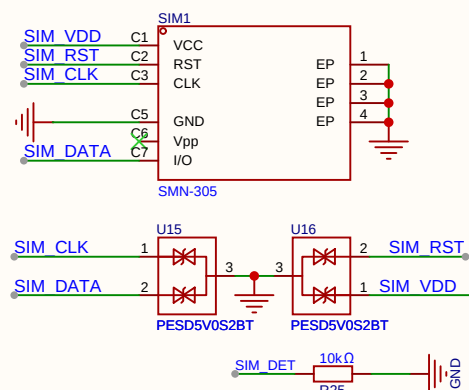


天线

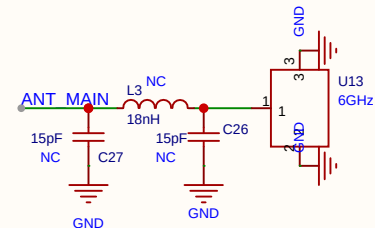


原理图	Schematic1			创建日期	2026-07-23
				更新日期	2026-07-30
板子	Board1			图页	4G模块
绘制	New Project_2026-07-19_11-10-43				
审阅					
		版本	尺寸	页 4 共 6	
		V1.0	A4	嘉立创EDA	


整版5V供电

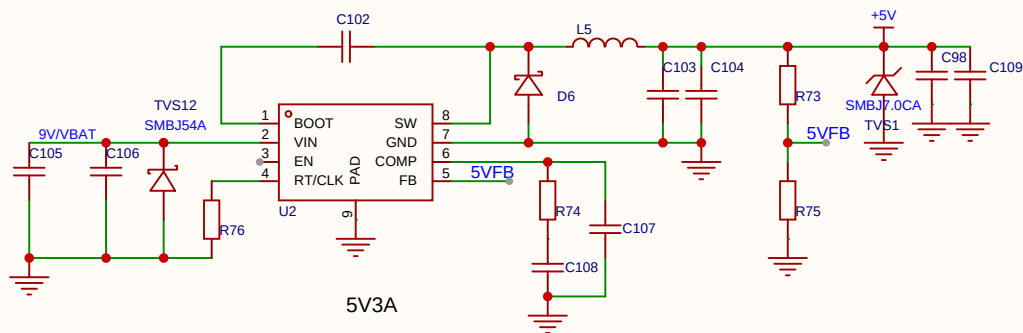

4G模块供电

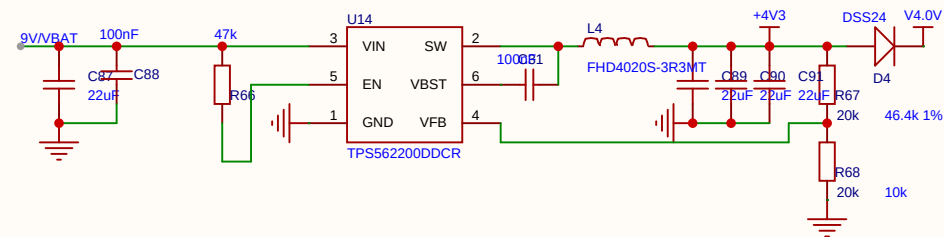

电池充电

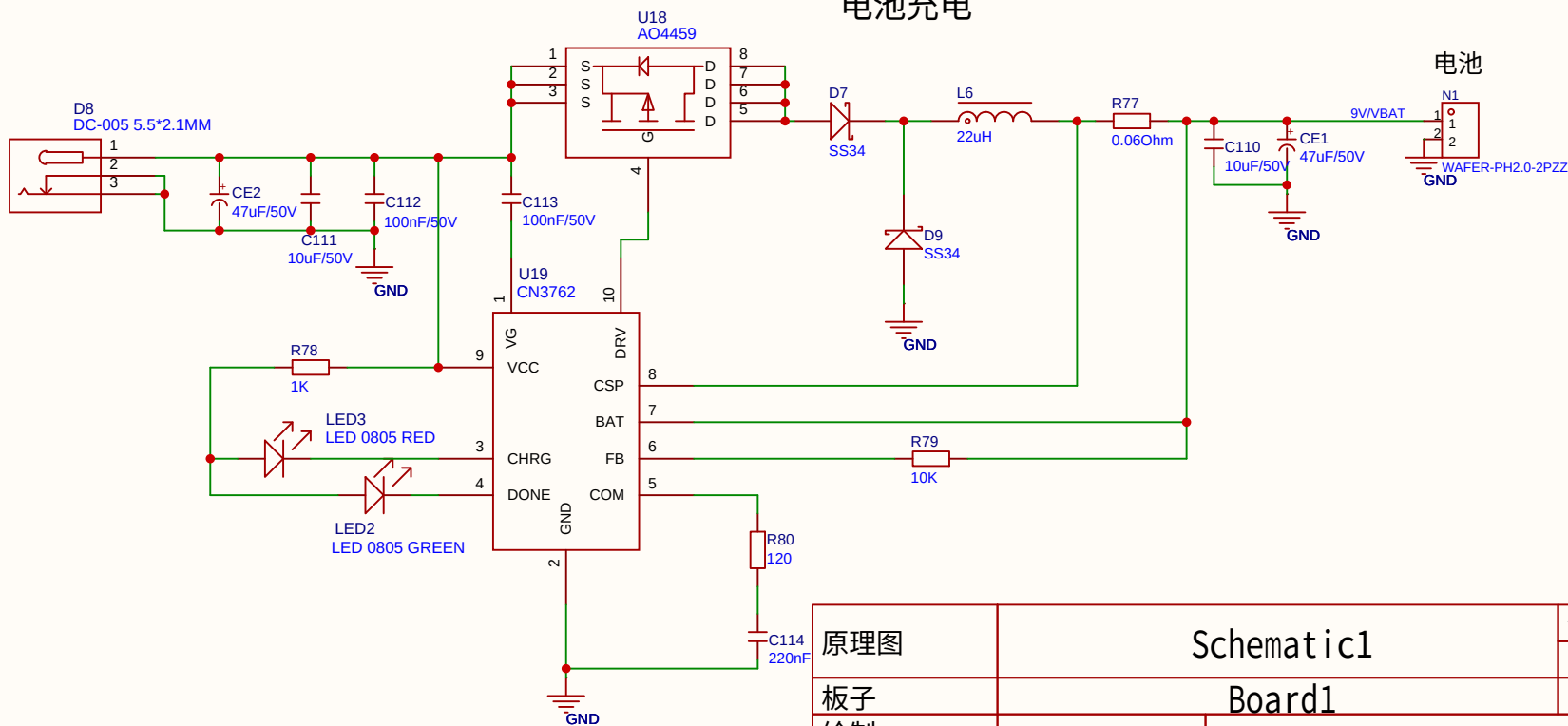

原理图	Schematic1			创建日期	2026-07-30
板子	Board1			更新日期	2026-08-08
绘制		New Project_2026-07-19_11-10-43			
审阅					
		版本	尺寸	页 5 共 6	
嘉立创EDA		V1.0	A4	嘉立创EDA	

1						2						3						4						5						6					
A																																			
B																																			
C																																			
D																																			
原理图												Schematic1												创建日期				2026-07-30							
																								更新日期				2026-07-30							
板子												Board1												图页				P2							
绘制												New Project_2026-07-19_11-10-43																							
审阅																																			
												版本				尺寸				页 6 共 6															
												V1.0				A4				嘉立创EDA															
1						2						3						4						5						6					